CombinationalLoop-ParityBit-HLS: Quiz Solution

www.highlevel-synthesis.com

The following figure shows the structure of the balanced three.

It has $\log_2 1024 = 10$ levels. And (1024-1) = 1023 XORs.

