

To enable the left-hand side display, we should apply 0 on W4 pin

To disable the others, V4, U4 and U2 should receive the logic value 1.

And the code on the data pins is 0b10010010


Control  
Signals

U2	U4	V4	W4
1	1	1	0

0b1110

Data  
Signals

DP	CG	CF	CE	CD	CC	CB	CA
V7	U7	V5	U5	V8	U8	W6	W7
1	0	0	1	0	0	1	0

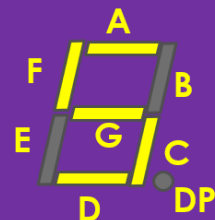

<https://highlevel-synthesis.com/>