

An 8x3 binary encoder gets an 8-bit input and returns a 3-bit output. The following function implements an 8x3 encoder using a switch-case statement. Note that only one bit of the encoder input can have the value of 1.

```
void encoder8x3(ap_int<8> a, ap_int<3> &d) {  
  
    switch(a) {  
        case 0b00000001:  
            d = 0b000;  
            break;  
        case 0b00000010:  
            d = 0b001;  
            break;  
        case 0b00000100:  
            d = 0b010;  
            break;  
        case 0b00001000:  
            d = 0b011;  
            break;  
        case 0b00010000:  
            d = 0b100;  
            break;  
        case 0b00100000:  
            d = 0b101;  
            break;  
        case 0b01000000:  
            d = 0b110;  
            break;  
        case 0b10000000:  
            d = 0b111;  
            break;  
        default:  
            d = 0b000;  
            break;  
    }  
}
```