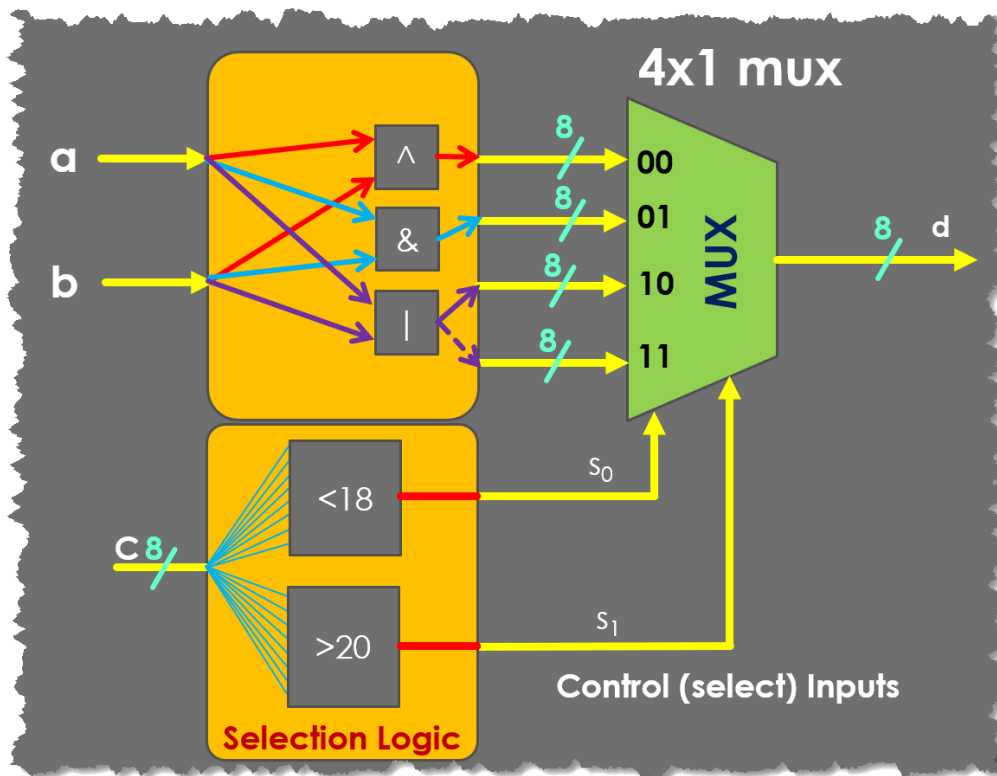


The following figure shows the circuit structure of the if-else statement in the quiz question.



If  $c$  is less than 18 then  $S_0 = 1$  and  $S_1 = 0$ , or the select input is "01". Therefore, the  $(a \& b)$  function is connected to the output.

If  $c$  is greater than 20 then  $S_0 = 0$  and  $S_1 = 1$ , or the select input is "10". Therefore, the  $(a | b)$  function is connected to the output.

Otherwise,  $S_0 = 0$  and  $S_1 = 0$  or the select input is "00". Therefore, the  $(a \wedge b)$  function is connected to the output.