CombinationalLoop-ParityBit-HLS: Quiz Solution

www.highlevel-synthesis.com

This file is a resource of the Udemy course: Digital System Design with High-Level Synthesis for FPGA: Combinational Circuits https://www.udemy.com/course/hls-combinational-circuits/?referralCode=8D449A491B9F4582DDEF

The following figure shows the structure of the balanced three.

It has $\log_2 1024 = 10$ levels. And (1024 - 1) = 1023 XORs.

