
Combinational Loop Definition: Quiz Solution

www.highlevel-synthesis.com

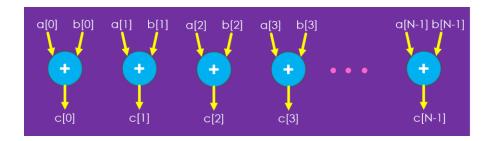

A *for*-loop can represent this dataflow graph. However, to execute iterations in parallel, adding the unrolling compiler directive is required.